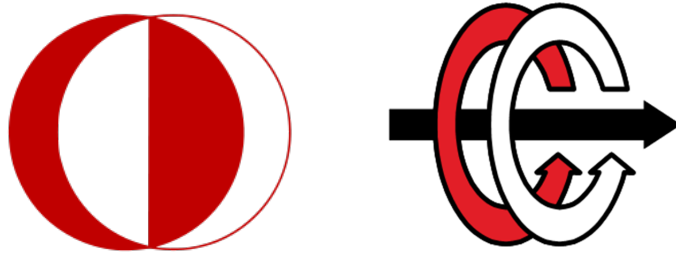


# **EE462 Spring 2016**

## **Project 0**

DC Motor Drive and Analysis

March 2017



Middle East Technical University

Electrical and Electronics Engineering Department

JeanPiere Demir

# 1 Brief Explanation

These report will try to explain and give information about DC Motor drive and analysis . The wanted specific details are,

- A short info about the motor (voltage, current, power ratings etc.)
- Short info about the power source and control system
- Graphs showing acceleration curve from stationary to rated speed
- Start-up current graphs
- Produced torque during start-up

# 2 Results

In that project, Firstly I used Chopper-Fed DC Motor Drive Example, and after thinking about Project-0 ,I decided, I will use H-bridge topology due to it is Project 0 and I can test which drive I want.

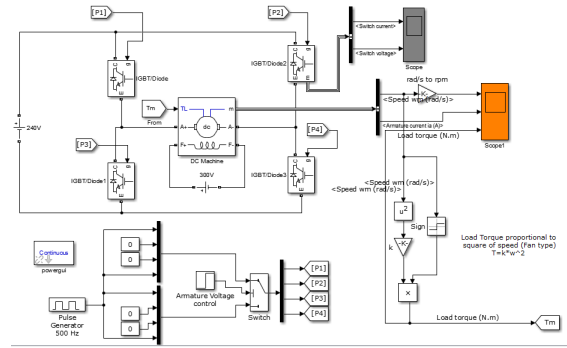


Figure 1: Simulink Diagram of H-Bridge Controlled DC Motor

## DC Motor Properties

I looked motor properties from Simulink DC Motor block, and properties are,

- 240V
- Nominal 15A (Maximum 30A)
- $\approx 240 * 15 = 3.6 kW$
- 300V field voltage
- 5 HP

-While looking and testing different motor selection, I realised that when I decreased the voltage of the field, field current was weakening .So,

- Induced Voltage ( $E_a$ )  $\downarrow \rightarrow$  Rotor Current ( $I_a$ )  $\uparrow \rightarrow$  Motor Torque ( $T_m$ )  $\uparrow$

Finally, when motor torque increased our acceleration will increase, so our speed will increase. Then our induced voltage will increase and hopefully our system will be again in steady-state .[2]

-About HP calculation,

$$HP = (\text{Speed(Rpm)} * \text{Torque}) / 5252$$

$$T = 15 \text{ Nm or}$$

$$HP = (\text{Voltage} * \text{Current} * \text{Efficiency}) / 746$$

$$I = 15.5 \text{ A (If we assume efficiency is 100)}$$

### Power Source and Control Explanation

The system consist of ,

- Power Source Part
- Motor Drive Part
- Control Part(To obtain closed-loop control),

240 V DC power supply used to feed the motor, and to control the DC motor I used H-Bridge topology. H-Bridge topology has four switching element and sometimes called as "Full Bridge". In contrast to MatLab SimScape Power System (power<sub>Hbridge</sub>) example I used IGBT switches instead of BJT.

As a machine I used Wound winding DC machine, and it is torque loaded. The torque value calculated via,

$$\text{Torque} = k * (\text{speed}^2)$$

### Graphs

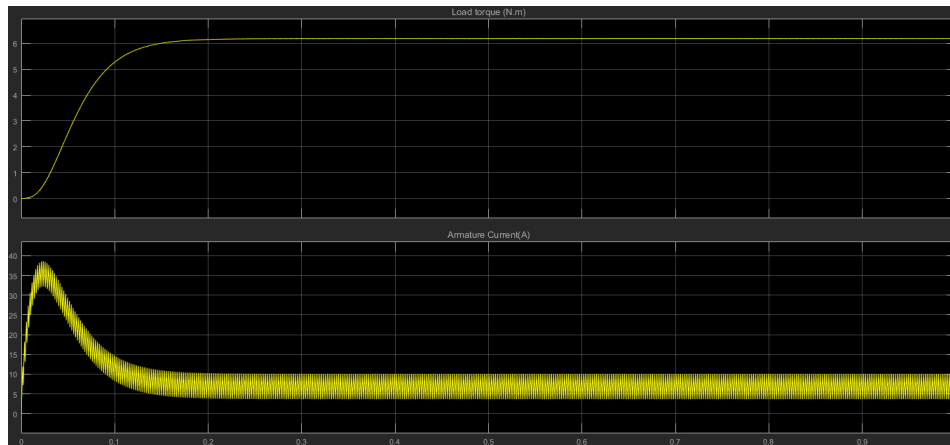


Figure 2: Torque and Current Graphs of DC Motor Drive

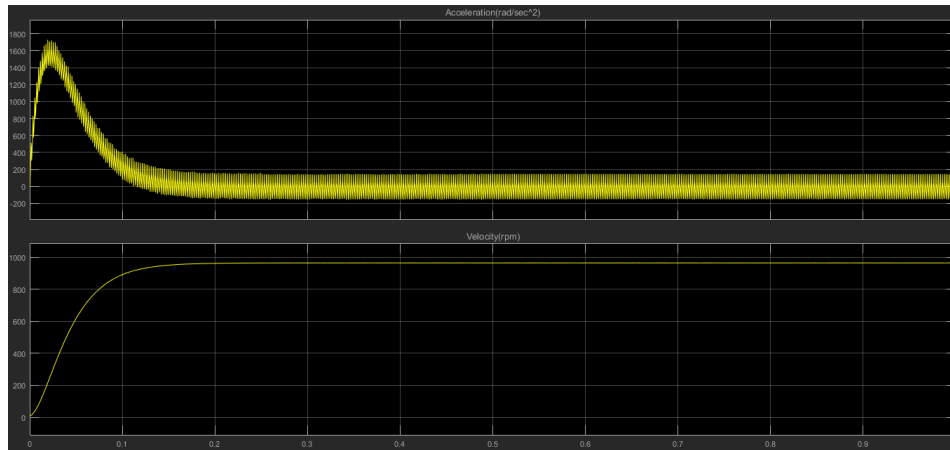


Figure 3: Acceleration and Velocity Graphs of DC Motor Drive

## References

- [1] Gilbert Sybille *Hydro-Quebec Transmission Company*. SimScape Power Systems Examples, MathWorks
- [2] <https://www.quora.com/Why-do-we-decrease-the-field-current-in-a-DC-shunt-motor-by-to-increase-the-speed-and-mechanical-output-power> *Quora*. (Loren Rademacher answer..)
- [3] <http://electrical-engineering-portal.com/5-most-common-motor-load-types> *Portal*. (Edward answer..)